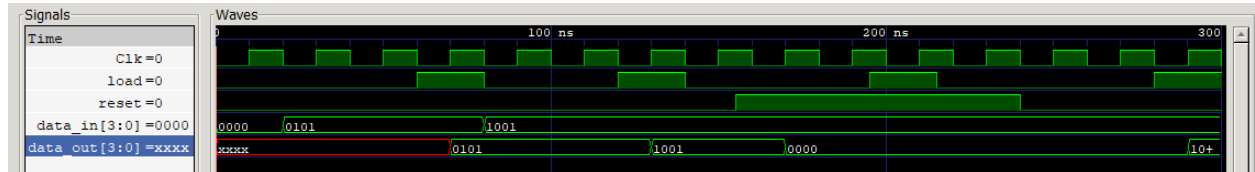



1. Write the use of enable and reset signal.

The enable signal is used to enable the shifting in shift registers, while the reset signal is used on both parallel and shift registers to set the register back to 0


Task 1:



Task 3:

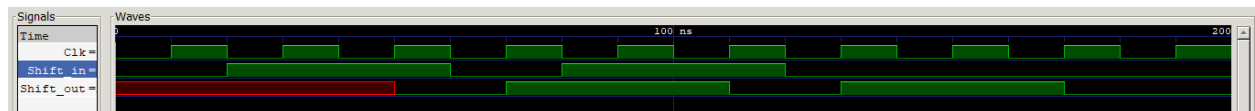

Task 4:

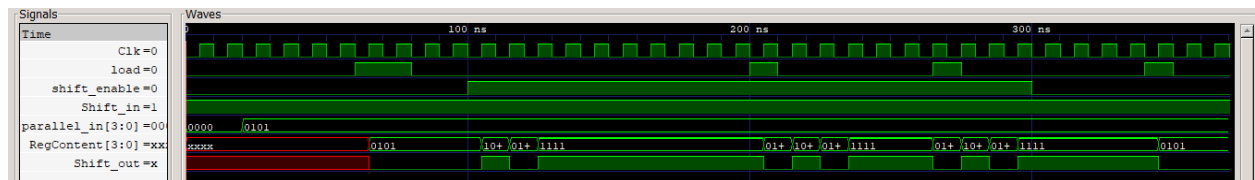

Task 5:

